



Dept. of Computer Science & Engineering

Course Code: CSE-2324

Course Title : Digital Logic Design Lab

Submitted by:

Name: Farida Nusrat

ID: C201242

Semester: 3rd

Section: 3AF

Contact: 01303994149

Email: c201242@ugrad.iiuc.ac.bd

Department of CSE, IIUC

Submitted to:

Mrs. Subrina Akter, Assistant
Professor, Dept. of CSE, IIUC

SIGN:

Farida Nusrat

SUBMISSION: 24-10-21

Experiment No: 08

Experiment Name: Implement 3 bit binary to octal decoder


Required tools:

- IC 74138
- Wires
- LED
- Electronic Workbench Software

Turth Table:

A	B	C	D₀	D₁	D₂	D₃	D₄	D₅	D₆	D₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

IC level diagram:

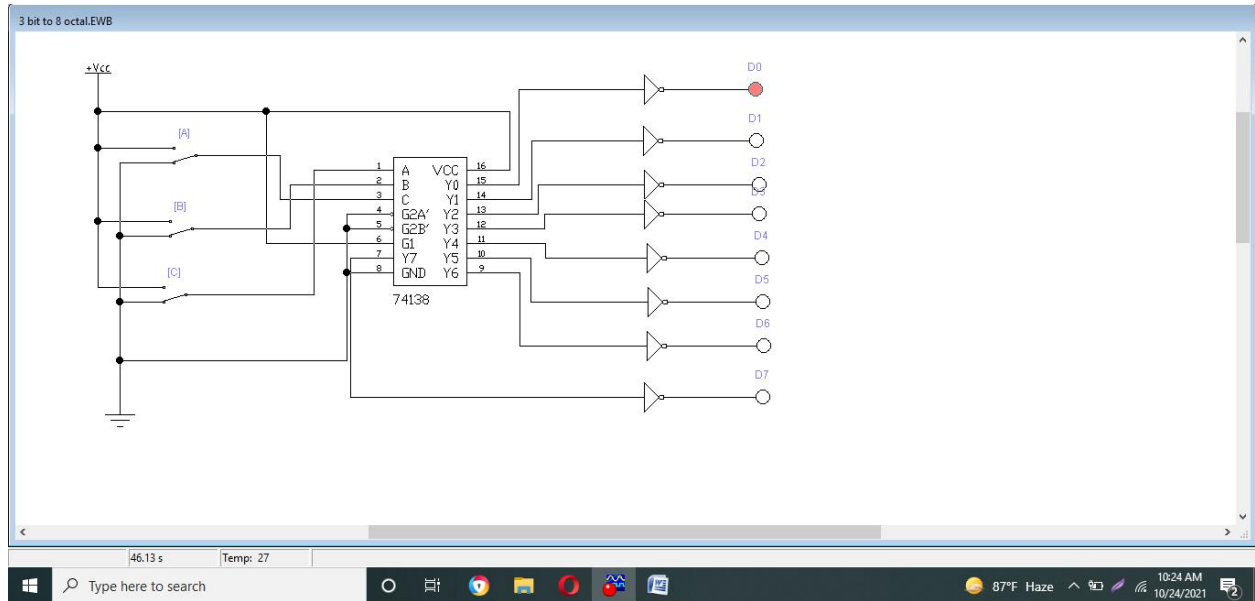

Result Discussion:

3-bit binary numbers at the input is converted to eight digits at the output (which is equivalent to octal number system). At a given time only one output is low and all other outputs will be high.

Any problem arises:

No.

What Have I learnt :

I have learn some how simple inputs of ones and zeros can be used to store information for output.