



## ***Dept. of Computer Science & Engineering***

**Course Code:** CSE-2324

**Course Title** : Digital Logic Design Lab

### **Submitted by:**

***Name:*** Farida Nusrat

***ID:*** C201242

***Semester:*** 3<sup>rd</sup>

***Section:*** 3AF

***Contact:*** 01303994149

***Email:*** [c201242@ugrad.iiuc.ac.bd](mailto:c201242@ugrad.iiuc.ac.bd)

***Department of CSE, IIUC***

### **Submitted to:**

Mrs. Subrina Akter, Assistant  
Professor, Dept. of CSE, IIUC


**SIGN:**

Farida Nusrat

**SUBMISSION:** 12-09-21
 
## **Experiment No: 04**

**Experiment Name** : : Implementation of half adder circuit diagram for 2 inputs.



### **Required tools:**


- XOR 7486, AND 7408
- Wires
- LED
- Electronic Workbench Software
- Switches
- Voltage
- Ground

### **Half Adder Truth Table:**

$A(Input)$	$B(Input)$	$S$	$C$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0

## Logic Circuit:

## IC level diagram:

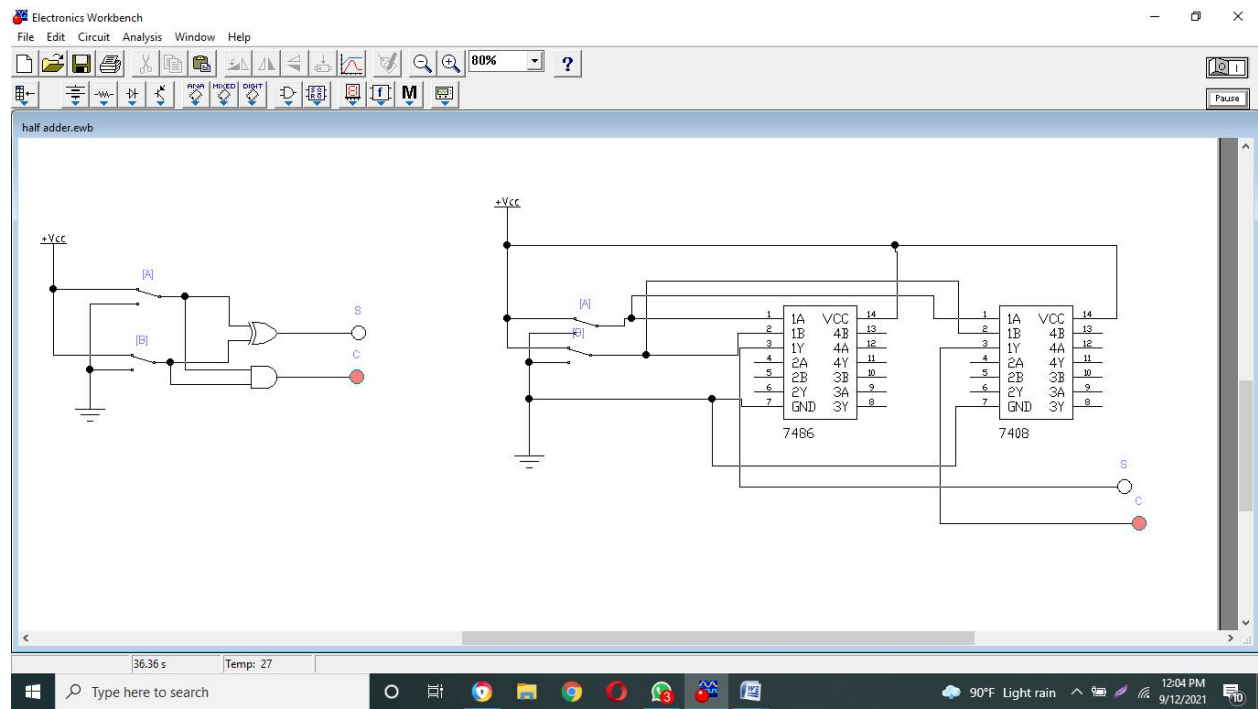

## Result Discussion:

*The experiments are verified and it show the appropriate results for the fundamental logic circuit.*

*Any problem arises:*No.

## *What Have I learnt:*

*I have learn some how simple inputs of ones and zeros can be used to store information for output.*