



## ***Dept. of Computer Science & Engineering***

**Course Code:** CSE-2324

**Course Title** : Digital Logic Design Lab

### **Submitted by:**

***Name:*** Farida Nusrat

***ID:*** C201242

***Semester:*** 3<sup>rd</sup>

***Section:*** 3AF

***Contact:*** 01303994149

***Email:*** [c201242@ugrad.iiuc.ac.bd](mailto:c201242@ugrad.iiuc.ac.bd)

***Department of CSE, IIUC***

### **Submitted to:**

Mrs. Subrina Akter, Assistant  
Professor, Dept. of CSE, IIUC

**SIGN:**

Farida Nusrat

**SUBMISSION:** 05-09-21

## **Experiment No: 03**

**Experiment Name** : Design circuit to verify DE morgan's law for two variable using only nand and nor gate

### **Required tools:**


- NOR 7402, NAND 7400
- Wires
- LED
- Electronic Workbench Software
- Switches
- Voltage
- Ground

### **NOR Turth Table:**

$A(Input)$	$B(Input)$	$A'$	$B'$	$(A+B)'$ (OUTPUT)	$(A'*B')$ (OUTPUT)
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

## Logic Circuit:

## IC level diagram:

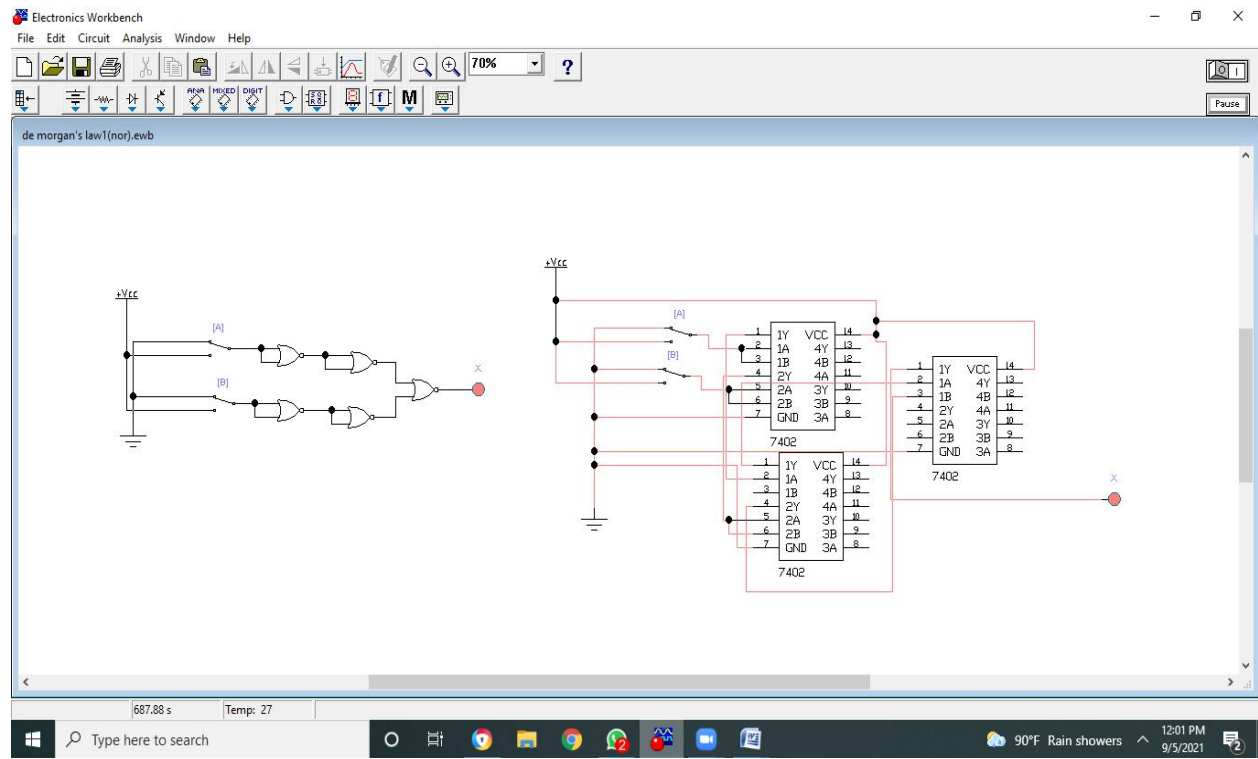


## NAND Turth Table:

$A(\text{Input})$	$B(\text{Input})$	$A'$	$B'$	$(A*B)'$ (OUTPUT)	$(A'+B')$ (OUTPUT)
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

## Logic Circuit:

## IC level diagram:

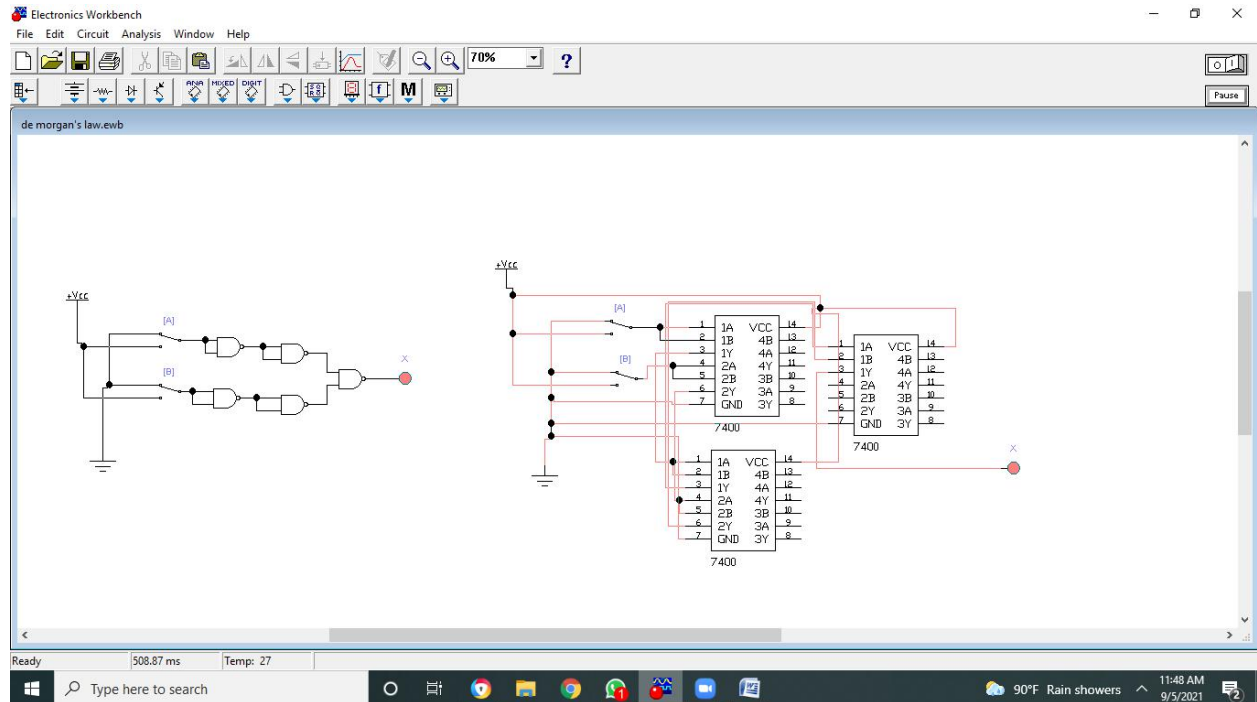

## Result Discussion:

*The experiments are verified and it show the appropriate results for the fundamental logic circuit.*

## Any problem arises:

No.

## What Have I Learnt:

*I have learn some how simple inputs of ones and zeros can be used to store information for output.*

